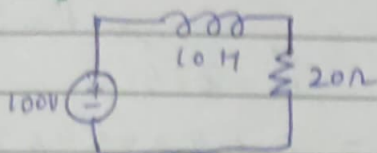


Assignment -3

A1)



$$at \quad t = 0.5s$$

$$t = 0.5s$$

$$L \frac{di}{dt} + i \times 20 = 100$$

$$\frac{di}{dt} + 2i = 10$$

$$i e^{2t} = \int 10 e^{2t} dt + c$$

$$i e^{2t} = \frac{10}{2} e^{2t} + c$$

$$at \quad t=0, \quad i=0 \Rightarrow c = -5$$

$$i = 5(1 - e^{-2t}) \text{ A}$$

$$at \quad t = 0.5s$$

$$i = 5(1 - e^{-1}) \approx 3.1606028 \text{ A}$$

$$(a) \quad p_{in} = i V_0 = 500(1 - e^{-1}) = 316.06028 \text{ W} \quad \uparrow \textcircled{1}$$

$$(b) \quad P_R = i^2 R = 500(1 - e^{-1})^2 = 199.7882 \text{ W} \quad \uparrow \textcircled{2}$$

~~Difference b/w a & b is stored in~~
~~the inductor is the sum of the energy stored~~
~~in inductor and heat ener~~

~~Some power is stored in~~

Difference b/w a & b is the ~~extra~~ power that is stored in inductor


$$\rightarrow P_{\text{stored}} = \frac{d}{dt} \left(\frac{1}{2} Li^2 \right) = \frac{d}{dt} \left(\frac{1}{2} \times 20 \times (5(1 - e^{-2t}))^2 \right) = 116.272074 \text{ W}$$

we can see that $\textcircled{2} + \textcircled{3} = \textcircled{1}$

\therefore Our statement is proved

\uparrow
 $\textcircled{3}$

A2)

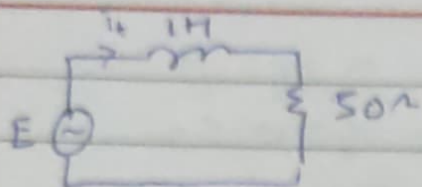

$$E = 141 \sin 314t$$

$$f = 50 \text{ Hz}$$

$$\omega = 314$$



$$(i_+) = \frac{141}{\sqrt{(50)^2 + (314)^2}} \approx 0.443457624$$

$$Z = \sqrt{(50)^2 + (314)^2}$$

$$= 317.955972$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \tan^{-1}(2\pi)$$

$$\approx 80.9569389^\circ$$

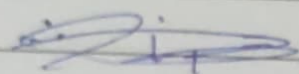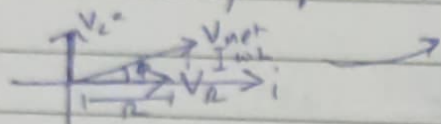


$$i_t = (i_+) \sin(314t - \phi)$$

$$i_t = \frac{141}{\sqrt{(50)^2 + (314)^2}} \sin(314t - 80.9569389^\circ)$$

$$i_t = (0.443457624) \sin(314t - \tan^{-1}(0.28))$$

$$80.9569389^\circ$$

A2)

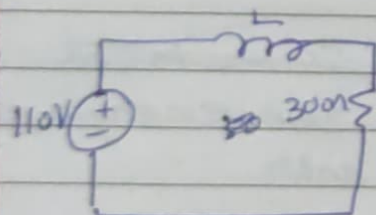

$$t = 0.002 \text{ s}$$

$$at \quad \tau = 63.2 \% \text{ of } i_0$$

$$(a) \quad \tau = 0.002 \text{ s} \quad (at \quad \tau = 63.2 \% \text{ of } i_0)$$


$$(b) \quad \tau = \frac{L}{R} = 0.002$$

$$L = 300 \times 0.002 = 0.6 \text{ H}$$


$$(c) \quad at \quad t = \infty, \quad i = i_0 = \frac{110}{300} = \frac{11}{3} \approx 0.3667 \text{ A}$$

$$(d) \quad \frac{di}{dt} = \frac{i_0}{\tau} e^{-t/\tau} \quad \therefore \left. \frac{di}{dt} \right|_{t=0} = \frac{V_0}{R} = \frac{110}{0.6} = 183.333 \text{ A/s}$$

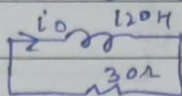A4) at $t=0 \Rightarrow i_0 = 5A$ and ~~circuit~~ circuit was



at $t > 0 \Rightarrow$ circuit was

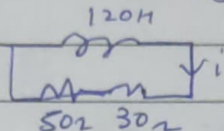

(Discharging circuit with $i(0) = 5A$)

$$\therefore i = i_0 e^{-t/\tau} \quad \text{where } \tau = \frac{120}{280} = 1.5s$$

$$\rightarrow \text{and } i_0 = 5A$$

$$\therefore i = 5e^{-\frac{2t}{3}}$$

req $t \Rightarrow$ at $t=0 \Rightarrow i = 5A$

at $t = \tau \Rightarrow i = 1.0A$


$$\therefore \downarrow$$

$$e^{-t/\tau} = \frac{1}{5}$$

$$\frac{t}{\tau} = \ln 5$$

$$\tau = \tau \ln 5 \approx 2.41415686865s$$

A 5)

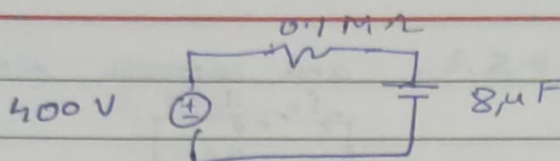

$$V_C = V_0 (1 - e^{-t/\tau})$$

$$\text{where } V_0 = 400 \text{ V}$$

$$\tau = 0.1 \times 10^6 \times 8 \times 10^{-6} \\ = 0.8 \text{ s}$$

$$\text{at } t = 0 \quad V_C = 0$$

$$\text{at } t = t \quad V_C = 300 \text{ V}$$

$$\therefore \text{req } t \Rightarrow \frac{300}{400} = 1 - e^{-t/\tau}$$

$$\therefore t = 0.8 \ln 4$$


$$\therefore t = 1.6 \ln 2 \approx 1.109035489 \text{ s}$$

$$E_t = \frac{1}{2} C V_t^2$$

$$E_{\infty} = \frac{1}{2} C V_0^2$$

$$\text{req Fraction} = \frac{E_t}{E_{\infty}} = \left(\frac{V_t}{V_0} \right)^2 = \frac{9}{16}$$
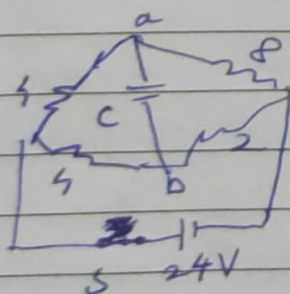
$$\therefore \text{req Fraction} = \frac{9}{16}$$



at in steady state
(blw a & b)
pd across C is 0
to pd Diffⁿ actions
a & b (V₀)

finding V₀ ↓


$$V_0 = 24 \times \frac{4}{4+8} - 24 \times \frac{4}{4+8}$$

$$= 24 \times 4 \left(\frac{1}{12} - \frac{1}{12} \right) = 8 \text{ V}$$

A 6)

\therefore pd developed across capacitor = 8V

Now ~~at instant~~ S is opened

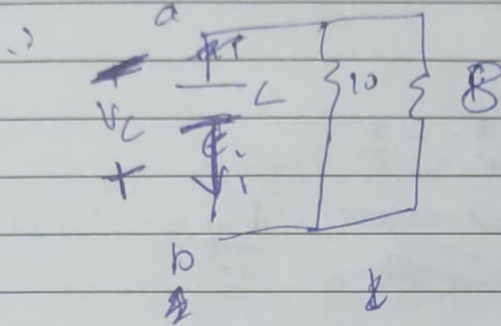


$$V_L = 8V$$

$$\therefore i = \frac{8}{\frac{1}{10} + \frac{1}{8}} = \frac{4 \times 80}{189}$$

$$= \frac{320}{9} \approx 35.5556 A$$

$$\therefore i \approx 35.5556 A$$

A7)

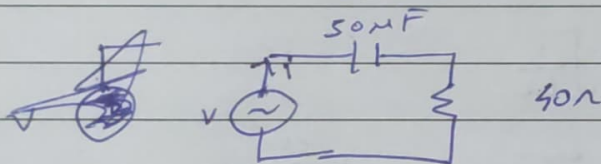


$$V = 283 \sin 314t$$

$$\omega C = 0.0157$$

$$i_0 = \frac{V_0}{Z}$$
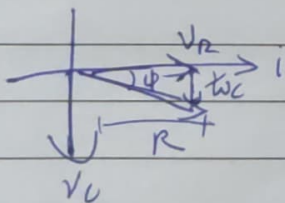
$$Z = \sqrt{(40)^2 + \left(\frac{1}{\omega C}\right)^2}$$



$$\tan \phi = \tan^{-1} \left(\frac{1}{\omega C R} \right)$$

$$\therefore i = i_0 \sin(\omega t + \phi)$$


$$\therefore i = \frac{V_0 \sin(\omega t + \phi)}{Z}$$

$$i = \frac{283}{\sqrt{1600 + \left(\frac{1}{0.0157}\right)^2}} \sin \left(\omega t + \tan^{-1} \left(\frac{1}{0.628} \right) \right)$$

$$i = 3.762659 \angle 72.24^\circ \sin (314t + 1.01004261622) A$$


\uparrow
in radians

48)

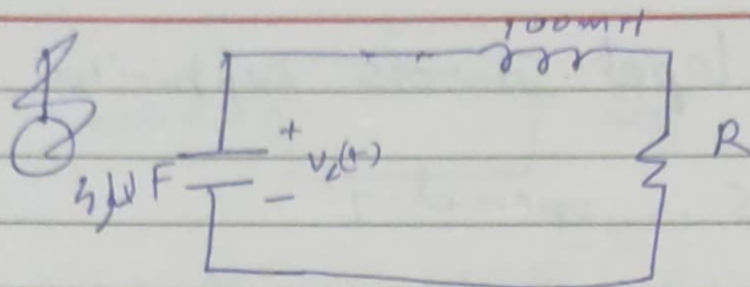

given \rightarrow
 $V_C(\oplus) = 300V$

(a) If $R = 0 \Omega$,

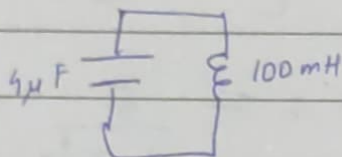

$$L \frac{d^2 q}{dt^2} = - \frac{q}{C}$$

~~$$m \omega^2 = -Kx$$~~
~~$$\omega^2 = \frac{K}{m}$$~~

$$\frac{d^2 q}{dt^2} = - \left(\frac{1}{LC} \right) q$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \sqrt{\frac{1}{LC}} = 2\pi f$$

$$\therefore f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$= \frac{1}{2\pi} \sqrt{\frac{1}{400 \times 10^{-4}}} = \frac{250}{4\pi} \sqrt{10}$$

$$= \frac{250 \sqrt{10}}{\pi}$$

$$\therefore f = \frac{250 \sqrt{10}}{\pi} = 251.64060522 \text{ Hz}$$

3

$$7 \frac{R^2}{4L^2} = \frac{1}{L} \Rightarrow R = 2\sqrt{L/L} = 2\sqrt{25 \times 10^3} = 100\sqrt{10}$$

$$\therefore R = 100\sqrt{10} = 316.227766017$$

1 Rough work

(b) If $R = 1 \Omega$,

$$q = \frac{q_0}{\omega} e^{-bt} \sin(\omega t + \alpha) \quad \text{where } \alpha = \tan^{-1}\left(\frac{\omega}{b}\right)$$

$$\text{Now } A = \frac{q / \omega \omega_0}{\omega} e^{-b t}$$

Now we are asked to find t when

$$\Delta \leq \frac{v_0}{20}$$

$$e^{-bt} \leq \frac{\omega}{10\omega}$$

$$e^{bt} \geq \frac{12\omega_0}{10\omega} + \frac{1}{b} \geq \frac{1}{b} \ln \frac{12\omega_0}{\omega}$$

Now if $t = nf$,

then

$$n \geq \frac{1}{\epsilon b} \frac{\ln(1/\alpha_0)}{\omega}$$

$$\therefore n = \left[\frac{1}{f_b} \ln \left(\frac{0.9}{0.1} \right) \right]$$

$$\therefore n = \lceil 0.4575 \rceil$$

$\therefore n=1$ if n is min. integer else $n=0.45 \neq 5$ cycle

where $b = 0.2 \text{ s}^{-1}$
 $\omega_0 = 500 \pi \text{ Hz}$
 $\omega = \sqrt{\omega_0^2 - b^2} \text{ Hz}$

and r_7 denotes
up to
ceil

And 美