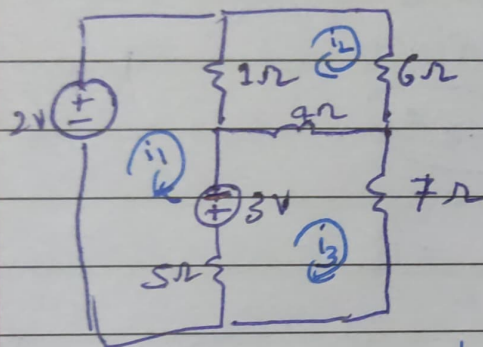


Basic Electronics (ECE 112) (Assignment-1)

A1)



$$\Rightarrow (-2) + (i_1 - i_2)1 + (-3) + (i_1 - i_3)5 = 0$$

$$6i_1 - i_2 - 5i_3 = 5 \quad (1)$$

$$\Rightarrow 6i_2 + 9(i_2 - i_3) + (i_2 - i_1)1 = 0$$

$$16i_2 - i_1 - 9i_3 = 0 \quad (2)$$

$$\Rightarrow 3 + 9(i_3 - i_2) + 7i_3 + 5(i_3 - i_1) = 0$$

$$3 + 21i_3 - 9i_2 - 5i_1 = 0 \quad (3)$$

by solving (1), (2), (3)

$$5i_1 + i_2 = 6i_1 - 5i_3$$

$$96i_1 - 80i_3 - 80 - 11i_5$$

$$695i_1 - 89i_3 = 80$$

$$495i_1 - 80 = i_3$$

$$6i_1 - i_2 - 5i_3 = 5$$

$$i_1 + 9i_3 = 16i_2$$

$$\cancel{3+2i_1} = 9i_2 + 5i_1$$

$$3+2i_1 \quad 3(7i_3) = 9i_2 + 5i_1 - 3$$

↓

$$6 - 18i_2 = 9i_2 + 5i_1 - 3$$

$$9 = 27i_2 + 5i_1$$

$$\frac{9-5i_1}{2} = 9i_2$$

$$\frac{4(1-3i_2)}{5} = i_1$$

$$\frac{2(1-3i_2)}{7} = i_3$$

$$6i_1 = 5 + 5i_3 + i_2$$

$$\frac{54}{5}(1-3i_2) = 5 + \frac{10}{7}(1-3i_2) + i_2$$

$$\left(\frac{7 \times 54 - 50}{35}\right)(1-3i_2) = 5 + i_2$$

$$328 - 984i_2 = 175 + 35i_2$$

$$\frac{328 - 175}{1019} = i_2 = \frac{153}{1019}$$

$$i_1 = \frac{9}{5} \left(\frac{560}{1019} \right)$$

$$= \frac{1008}{1019}$$

$$i_3 = \frac{2}{7} \left(\frac{560}{1019} \right)$$

$$= \frac{160}{1019}$$

$$i_1 = 153/1019$$

$$i_2 = 1008/1019$$


$$i_3 = 160/1019$$

$$i_1 = 1008/1019$$

$$i_2 = 153/1019$$

$$i_3 = 160/1019$$

A2)

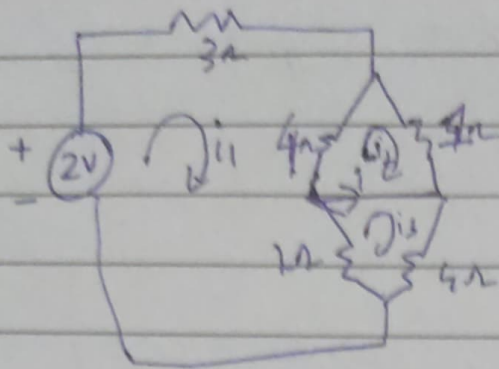

$$-2 + 3i_1 + 4(i_1 - i_2) + (i_1 - i_2) = 0$$

$$8i_1 - 4i_2 - i_3 = 2 \quad \text{--- (1)}$$

~~$$4i_1 + 4i_2 + i_3 = 2$$~~

$$i_2 + 4(i_2 - i_1) = 0$$

$$5i_2 = 4i_1 \quad \text{--- (2)}$$

$$4i_3 + (i_3 - i_1) = 0$$

$$5i_3 = i_1 \quad \text{--- (3)}$$

by solving (1), (2) & (3)

$$8i_1 - 4\left(\frac{4i_1}{5}\right) - \frac{i_1}{5} = 2$$

$$\frac{23i_1}{5} = 2$$

$$i_1 = \frac{10}{23} \text{ A}$$

$$i_3 = \frac{2}{23} \text{ A}$$

$$i_2 = \frac{8}{23} \text{ A}$$

~~$$i_1 + i_2 = i_3$$~~

$$\therefore i = i_3 - i_2$$


$$= \frac{2}{23} - \frac{8}{23}$$

$$= -\frac{6}{23}$$

$$\therefore i = -\frac{6}{23} = (-0.26086956521) \text{ A}$$


A-3)

(a) 4 eqⁿ(s) are required

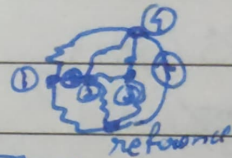

$\therefore 4 \text{ eqⁿs}$

(b) 5 eqⁿ(s) are required

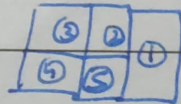


$\therefore 5 \text{ eqⁿs}$

(c) ~~earlier~~ I would have used Node analysis here, ~~now, and now~~ I earlier as well as now.


\therefore No My preferred method would not change because in Nodal analysis, ~~we directly~~ ~~we would easily~~ get node voltages, from which we can directly compute voltage but if we use ~~Nodal~~ Mesh analysis first I would calculate current through R resistor then voltage,

P.T.O.

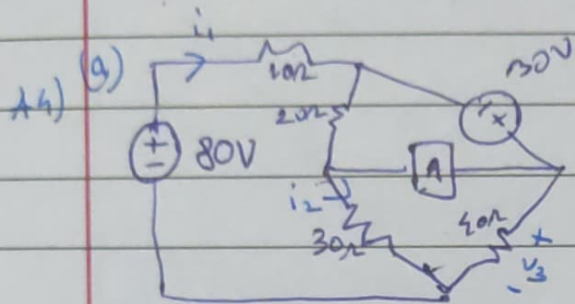So we obtain desired ~~desired~~ with lesser computation \therefore I would prefer Nodal analysis for this one as well.



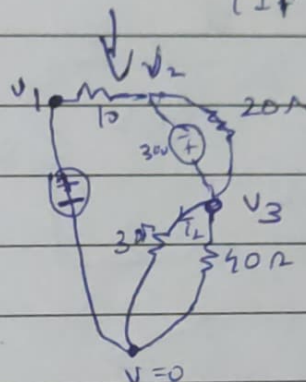Nodal analysis will be better
(if A \rightarrow shortcircuit)




\rightarrow clearly
 $v_1 = 80$ ✓

\therefore applying KCL at super Node v_2 & v_3

$$\downarrow \quad \frac{v_3}{30} + \frac{v_3}{40} + \frac{v_2 - 80}{10} = 0 \quad \text{--- (1)}$$

also $v_3 - v_2 = 30$ --- (2)
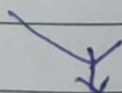
$$\frac{7v_3}{12} + v_2 - 80 = 0 \quad \text{--- (1)}$$




$$\frac{7v_3}{12} + (v_3 - 30) - 80 = 0$$

$$v_3 \left(\frac{7}{12} + 1 \right) = 110$$



$$v_3 = \frac{1320}{14}$$

$$i_2 = \frac{v_3}{30}$$
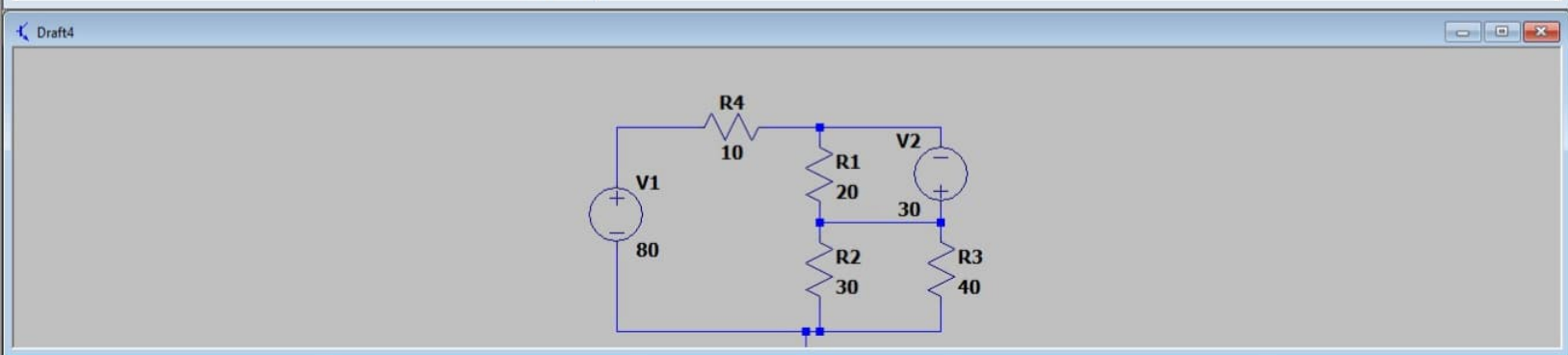
$$\Rightarrow i_2 = \frac{44}{14} \text{ A}$$



As) (a)

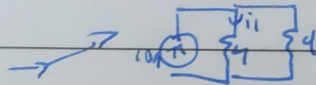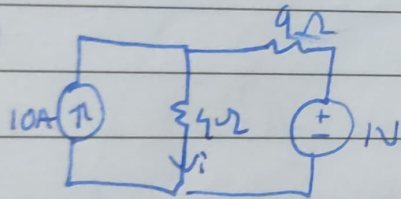

$$\Rightarrow i_1 = \frac{90}{13} \text{ A}$$





$$\Rightarrow i_2 = \frac{1}{13} \text{ A}$$

$$i = i_1 + i_2 = \frac{91}{13} \text{ A}$$

$$(b) \% \text{ Contribution} = \frac{i_2}{i} \times 100 = \frac{1/13}{91/13} \times 100 = \frac{100}{91} \% \approx 1.099\%$$

$$(c) \quad \frac{L}{13} = i \times \frac{9}{13} \Rightarrow i = \frac{1}{9} A$$

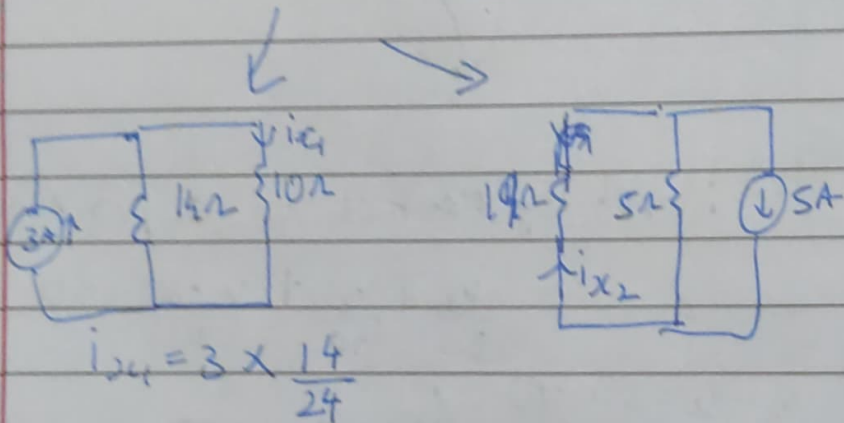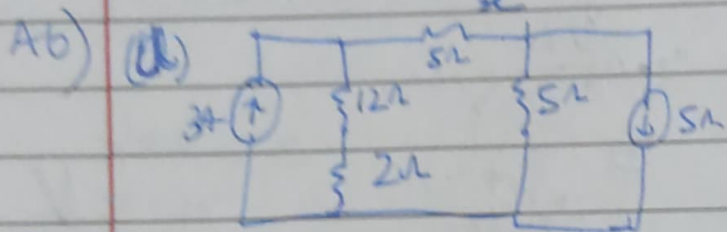\therefore if instead of $10 A$ $i_s = \frac{1}{4} A$ then i_v and i_x will contribute equally to i .



$$i_{x1} = 3 \times \frac{14}{24}$$


$$i_{x2} = 5 \times \frac{5}{24}$$

$$\begin{aligned} i_x &= (-i_{x1}) + (-i_{x2}) \\ &= -\left(\frac{42 + 25}{24}\right) = -\frac{67}{24} A \end{aligned}$$

(b)

$$\frac{42}{24} = + i_x \times \frac{5}{24}$$
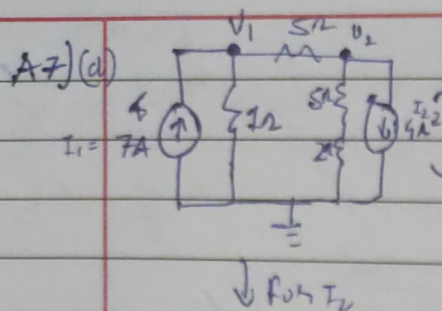
$$\therefore i_x = \frac{42}{5} = 8.4 A$$



$$\frac{v_1'}{1} + \frac{v_1' - v_2'}{5} = 7 \quad \Delta \quad \frac{v_2'}{7} + \frac{v_2' - v_1'}{5} = 0$$

$$6v_1' - v_2' = 35 \quad 12v_2' = 7v_1'$$

$$v_1' \left(6 - \frac{7}{12}\right) = 35 \rightarrow v_1' = \frac{12 \times 35}{65} = \frac{84}{13}$$

$$\frac{v_1''}{1} + \frac{v_1'' - v_2''}{5} = 0$$

$$4 + \frac{v_2''}{7} + \frac{v_2'' - v_1''}{5} = 0$$

$$6v_1'' = v_2''$$

$$4 + \frac{v_2''}{7} + v_1'' = 0$$

$$28 + 6v_1'' + 7v_1'' = 0$$

$$-\frac{28}{13} = v_1''$$

$$v_1' = v_1' + v_1''$$

$$v_1 = \frac{84 - 28}{13} = \frac{56}{13}$$

$$-\frac{6 \times 4}{13}$$

(b)

$$P_T = (i_1 + i_2)^2 \times 2$$

$$= \left(\frac{v_2'}{7} + \frac{v_2''}{7} \right)^2 \times 2 = \left(\frac{7}{13} + \frac{-24}{13} \right)^2 \times 2$$

$$P_1 = i_1^2 \times 2 = \left(\frac{7}{13} \right)^2 \times 2$$

$$= \left(\frac{-13}{13} \right)^2 \times 2$$

$$P_2 = i_2^2 \times 2 = \left(\frac{-24}{13} \right)^2 \times 2$$

$$\% \text{ Contribution of } 1 = \frac{P_1}{P_T} \times 100 = \left(\frac{70}{17} \right)^2 \approx 16.9550173\%$$

$$\% \text{ Contribution of } 2 = \frac{P_2}{P_T} \times 100 = \left(\frac{240}{17} \right)^2 \approx 235.29\%$$

$$\approx 199.307958478\%$$